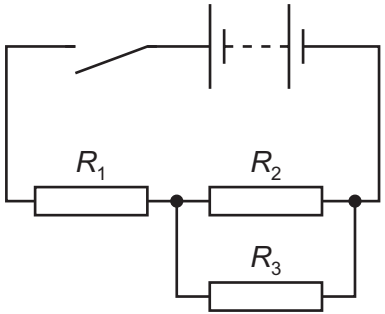
29 The diagram shows an arrangement of resistors in series and parallel.



Which equation is used to calculate the combined resistance of the resistors?

A $R_1 + \dfrac{R_2 + R_3}{R_2 \times R_3}$

B $R_1 + \dfrac{R_2 \times R_3}{R_2 + R_3}$

C $R_1 + \dfrac{1}{R_2 + R_3}$

D $R_1 \times \dfrac{R_2 + R_3}{R_2 \times R_3}$