28 Which statement describes how a diode operates in an electrical circuit?

A When the temperature increases, its resistance increases.

B When the current becomes too high, it melts and cuts off the current.

C It only allows current in one direction.

D It uses a low-current circuit to switch on a circuit carrying a much larger current.