

29 A number of identical resistors of resistance 10 Ω are arranged in circuits.

Which arrangement of resistors will give an overall resistance of 25 Ω?

A

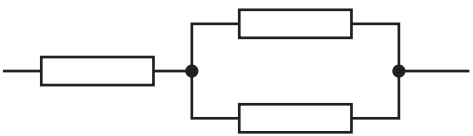

B

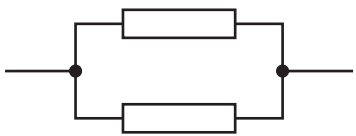

C



D

