
30 The circuit diagram shows a thermistor in a potential divider.

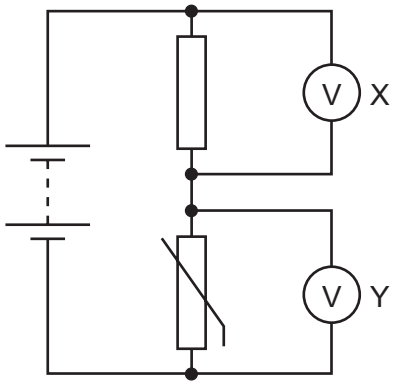Two voltmeters X and Y are connected in the circuit.



When the temperature of the thermistor increases, its resistance decreases.

As the thermistor becomes warmer, what happens to the reading on each voltmeter?

	reading on voltmeter X	reading on voltmeter Y
A	decreases	decreases
B	decreases	increases
C	increases	decreases
D	increases	increases