27 A cell passes a current of 2.0 A in a circuit for 30 s. In this time, the cell transfers 120 J of energy.

What is the electromotive force (e.m.f.) of the cell?

A 0.50 V **B** 1.5 V **C** 2.0 V **D** 8.0 V