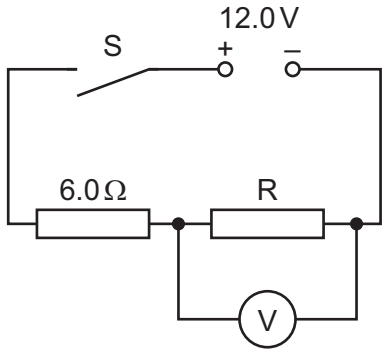
28 The diagram shows two resistors in series connected to a power supply.



The reading on the voltmeter is 3.0 V when the switch is closed.

What is the resistance of resistor R?

A 0.67 Ω **B** 1.2 Ω **C** 1.5 Ω **D** 2.0 Ω