29 Lamps can be connected in series or in parallel to a power supply.

What is an advantage of connecting the lamps in parallel rather than in series?

A All of the lamps can be switched on and off using the same switch.

B Fewer connecting leads are needed to make the circuit.

C When one lamp stops working, the others may continue to work.

D Less power is transferred from the supply.