

27 Which circuit contains a light-dependent resistor (LDR)?


A

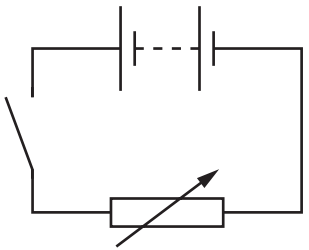

B

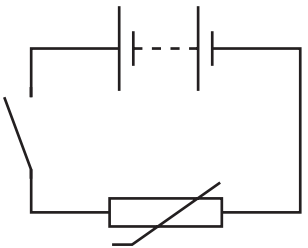

C

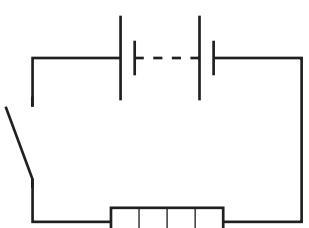

D

