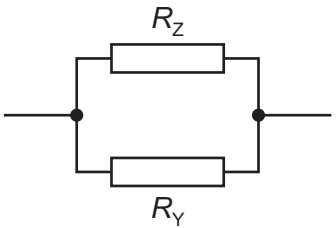
28 A teacher asks three students to write down an equation to determine the combined resistance R_C of resistors with resistances R_Y and R_Z.



Which students are correct?

student 1 $\frac{1}{R_C} = \frac{1}{R_Y} + \frac{1}{R_Z}$

student 2 $\frac{1}{R_C} = \frac{1}{R_Y + R_Z}$

student 3 $R_C = \frac{1}{R_Y} + \frac{1}{R_Z}$

A 1 and 2 **B** 1 only **C** 2 and 3 **D** 3 only