26 There is an electric current in a circuit with a battery. This question refers to the positive and negative terminals of the battery.

Which row correctly describes the directions of the conventional current and the electron flow in the circuit?

	direction of conventional current	direction of electron flow
A	from the negative to the positive terminal	from the negative to the positive terminal
B	from the negative to the positive terminal	from the positive to the negative terminal
C	from the positive to the negative terminal	from the negative to the positive terminal
D	from the positive to the negative terminal	from the positive to the negative terminal