28 A torch has a simple circuit with a 3.0 V battery and a lamp. There is a 20 mA current in the lamp.

How much energy is transferred to the lamp in 5.0 minutes?

A 0.30 J **B** 18 J **C** 60 J **D** 0.30 kJ