

29 In which circuit does the lamp light?


A

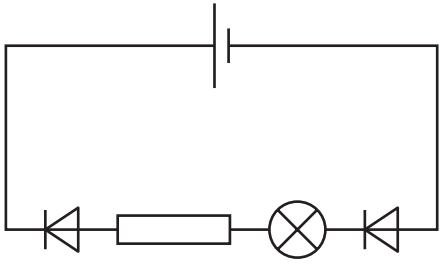

B

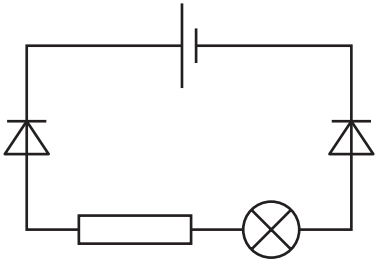

C

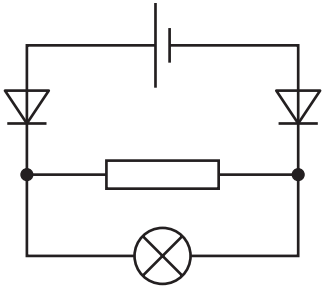

D

