

30 Which circuit shows possible correct values for the currents?


A

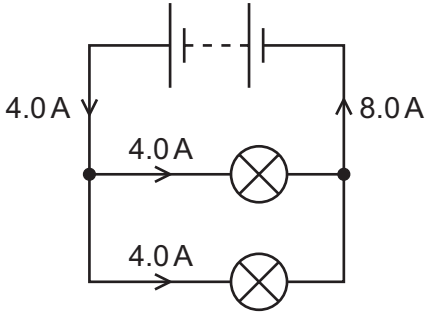

B

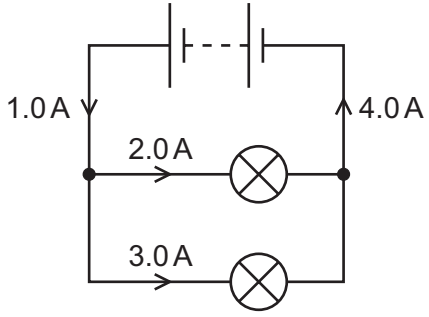

C

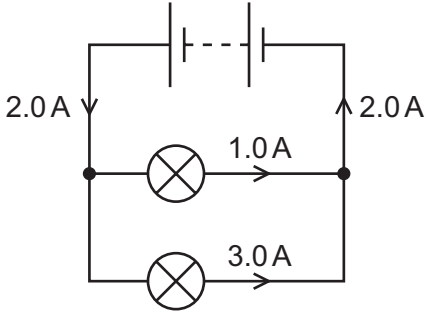

D

