

31 The circuit diagrams show circuits that can control the potential difference (p.d.) across a lamp.

Which circuit allows the p.d. across the lamp to be varied from 0 V to 6.0 V?


A

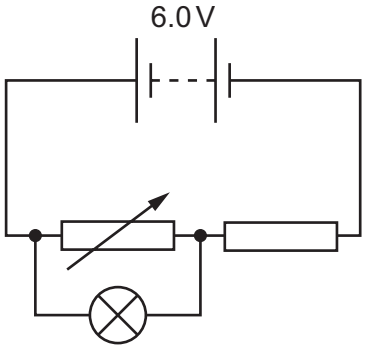

B

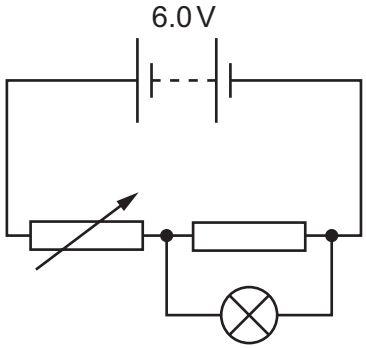

C

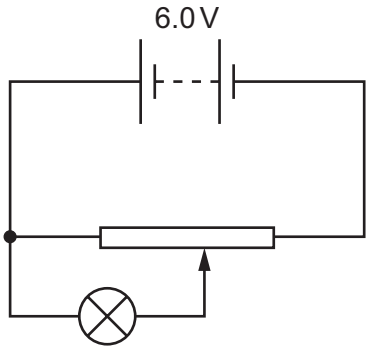

D

