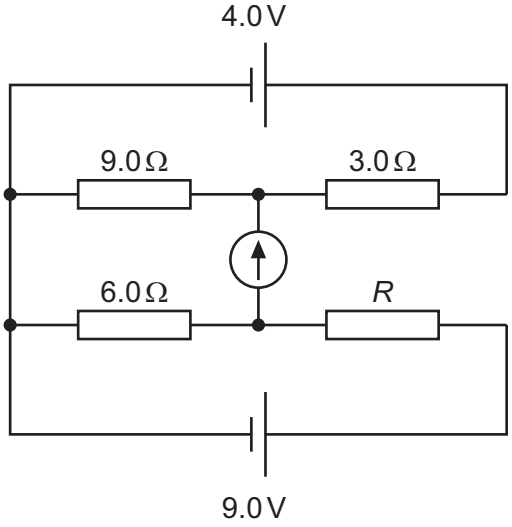
37 In the circuit shown, the cells have negligible internal resistance and the reading on the galvanometer is zero.



What is the value of resistor *R*?

A 2.0 Ω **B** 6.0 Ω **C** 12 Ω **D** 18 Ω