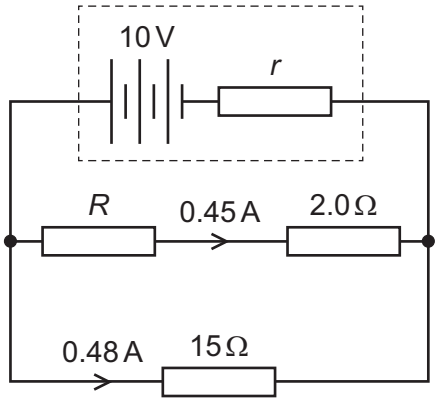
36 A battery of electromotive force (e.m.f.) 10 V and internal resistance r is connected to three resistors of resistances R, 2.0 Ω and 15 Ω, as shown. A current of 0.45 A is in the resistor of resistance 2.0 Ω and a current of 0.48 A is in the resistor of resistance 15 Ω.



What are the values of r and R?

	r/Ω	R/Ω
A	3.0	14
B	3.0	20
C	5.8	14
D	5.8	20