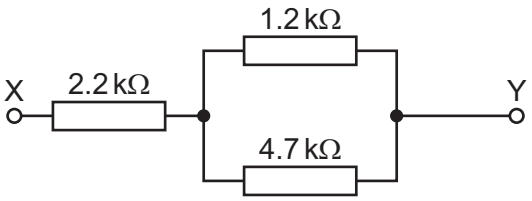
33 The diagram shows a network consisting of three resistors.



What is the combined resistance of the network between terminal X and terminal Y?

A 0.67 kΩ **B** 1.6 kΩ **C** 3.2 kΩ **D** 8.1 kΩ