34 A resistor dissipates 25 W of power when there is a potential difference (p.d.) of 4.0 V across it.

What is the resistance of the resistor?

A 0.16 Ω **B** 0.64 Ω **C** 100 Ω **D** 400 Ω