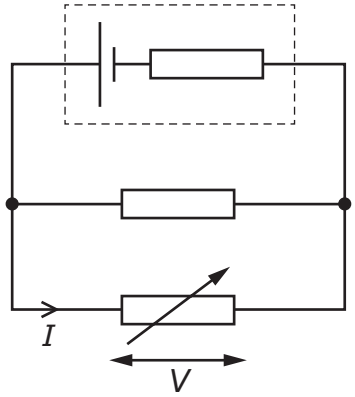
35 The diagram shows a cell with internal resistance connected in parallel with a fixed resistor and a variable resistor.



The resistance of the variable resistor is decreased.

What happens to the potential difference V across the variable resistor and the current I in the variable resistor?

	V	I
A	decreases	decreases
B	decreases	increases
C	increases	decreases
D	increases	increases