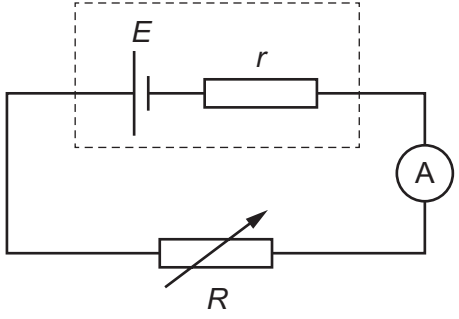
35 A cell has internal resistance r and electromotive force (e.m.f.) E. The cell is connected in series with an ammeter and a variable resistor of resistance R.



When R is 10 Ω the ammeter reads 0.3 A.

When R is 5 Ω the ammeter reads 0.4 A.

What is the value of E?

A 0.5 V **B** 2 V **C** 3 V **D** 6 V