36 The sum of the currents entering a junction in an electrical circuit is always equal to the sum of the currents leaving the junction.

Why is this?

A It is a consequence of the conservation of charge.

B It is a consequence of the conservation of electromotive force.

C It is a consequence of the conservation of energy.

D It is a consequence of the conservation of potential difference.