

37 In the circuits shown, the temperature remains constant.

In which circuit does the potential difference (p.d.) *V* increase with increasing light intensity?


A

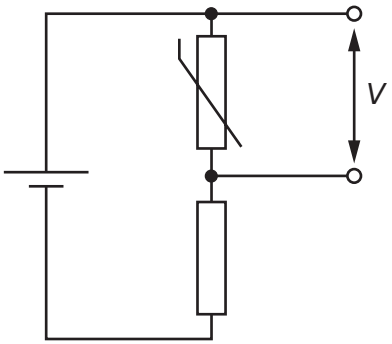

B

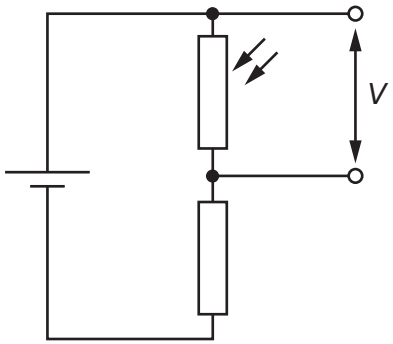

C

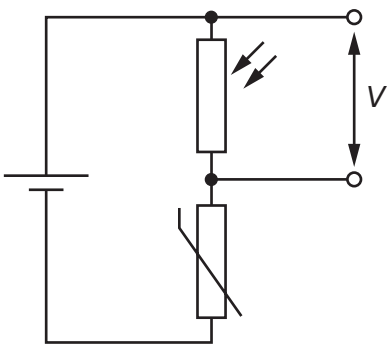

D

