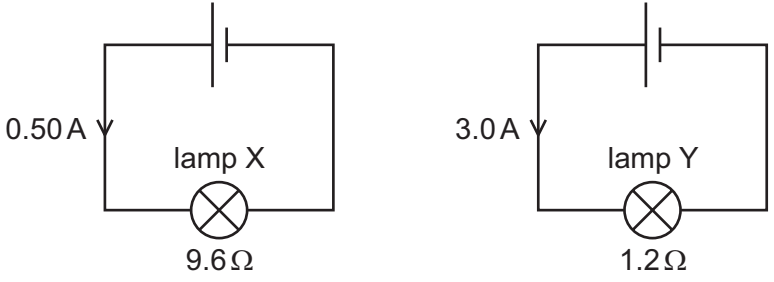
32 The circuit diagrams show two lamps X and Y each connected to a cell. The current in lamp X is 0.50 A and its resistance is 9.6 Ω. The current in lamp Y is 3.0 A and its resistance is 1.2 Ω.



What is the ratio $\frac{\text{power in lamp X}}{\text{power in lamp Y}}$?

A 0.22 **B** 0.75 **C** 1.3 **D** 4.5