
**37** A potentiometer circuit is used to determine the electromotive force (e.m.f.) $E_X$ of a cell. The circuit includes a second cell of known e.m.f. $E_0$ and negligible internal resistance, and a uniform resistance wire PQ of known length.

$E_X$ is less than $E_0$.


The movable connection J can be positioned anywhere along the length of the resistance wire.

Which circuit is suitable for determining $E_X$?


**A**

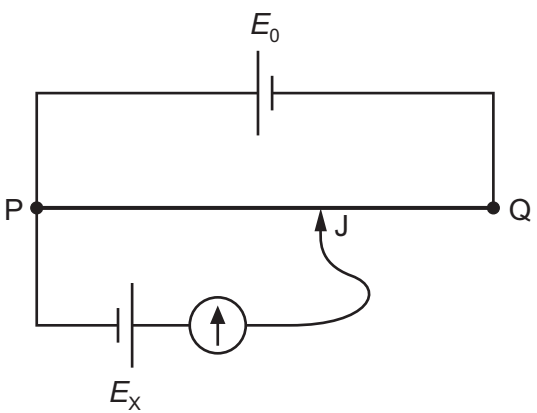


**B**

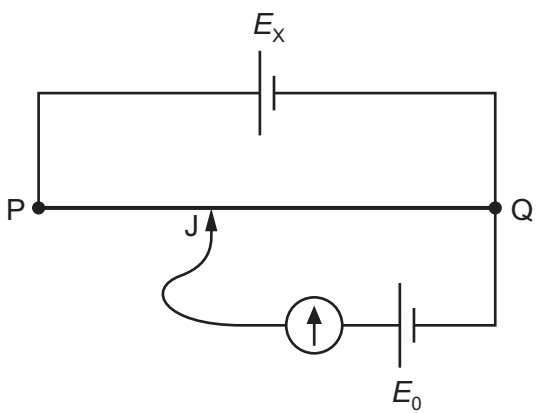


**C**

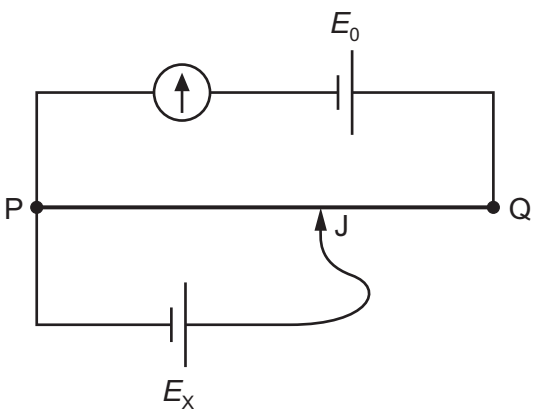


**D**

