
34 A fixed resistor and a filament lamp are connected in series to a power supply.

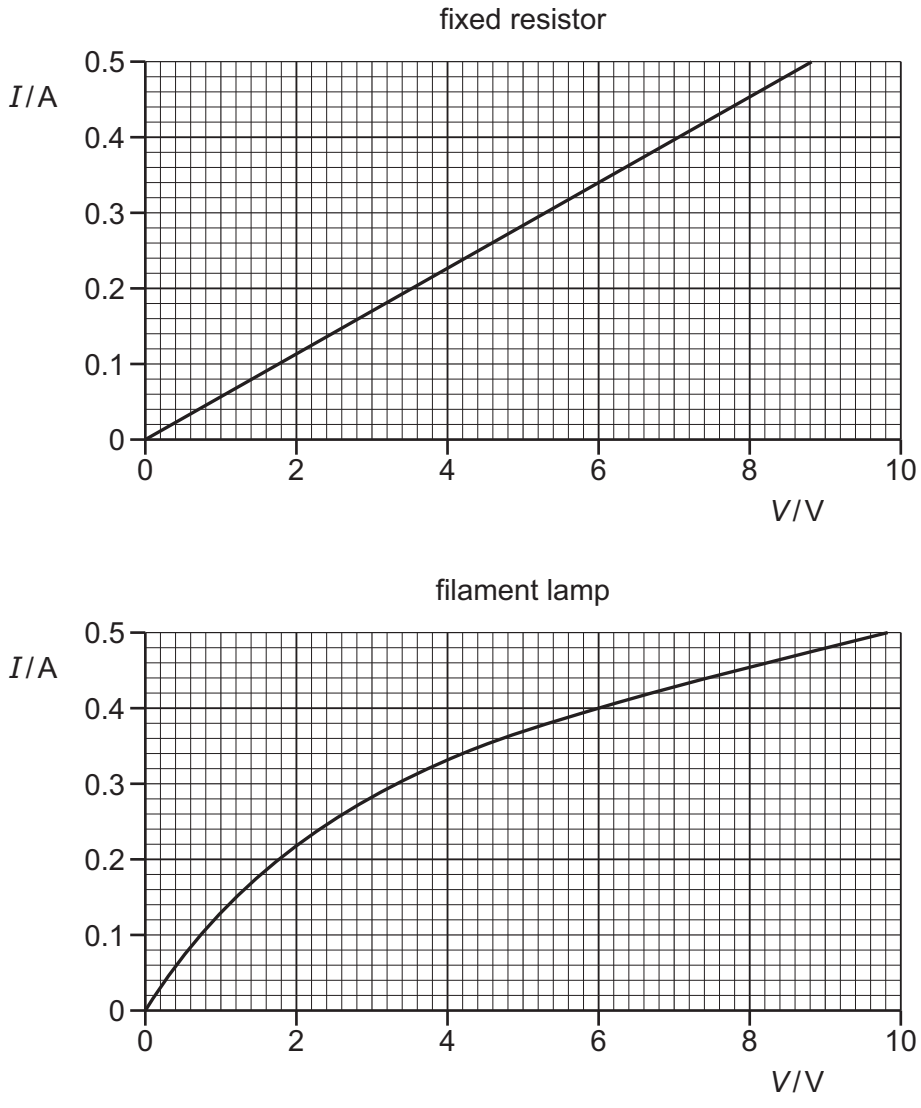The I–V characteristics for the two components are shown.



The current in the fixed resistor is 0.34 A.

What is the resistance of the filament lamp?

A 0.081 Ω **B** 12 Ω **C** 15 Ω **D** 18 Ω