36 The diagram shows the symbol for a component that may be used in an electrical circuit.



Which component is represented by this circuit symbol?

A buzzer

B electric bell

C loudspeaker

D microphone