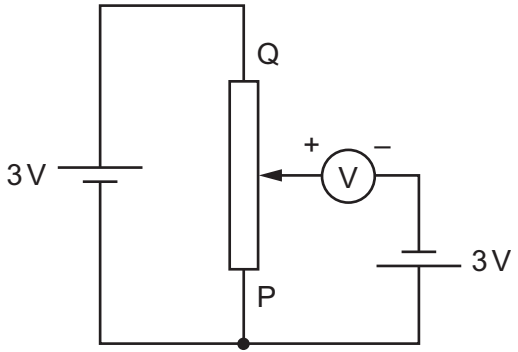
37 A voltmeter is connected into a circuit with the polarity shown.



The sliding contact is moved to end P of the potentiometer and then to end Q.

What are the two readings of the voltmeter?

	sliding contact at end P	sliding contact at end Q
A	0 V	3 V
B	0 V	6 V
C	3 V	3 V
D	3 V	6 V