31 A resistor of resistance R is connected across a cell of electromotive force (e.m.f.) E and negligible internal resistance.

Which single change to the circuit would lead to the largest increase in the power dissipated in the resistor?

A doubling the value of E

B doubling the value of R

C halving the value of E

D halving the value of R