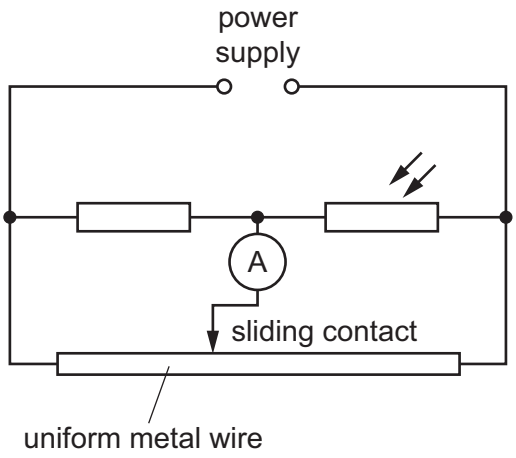
37 In the potentiometer circuit shown, the reading on the ammeter is zero.



The light-dependent resistor (LDR) is then covered and the ammeter gives a non-zero reading.

Which change could return the ammeter reading to zero?

A decreasing the supply voltage

B increasing the supply voltage

C moving the sliding contact to the left

D moving the sliding contact to the right