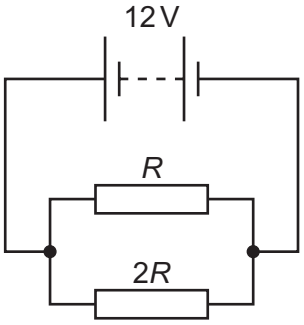
31 Two resistors of resistances R and $2R$ are connected in parallel with a battery of electromotive force (e.m.f.) 12 V and negligible internal resistance.



The total power dissipated by the two resistors is 36 W.

What is the value of R?

A 0.50 Ω **B** 2.7 Ω **C** 4.0 Ω **D** 6.0 Ω