
33 A cell of negligible internal resistance is connected in series with a thermistor, a fixed resistor and an ammeter.

The thermistor is placed in a beaker of water and the temperature of the water is slowly increased.


A graph of current I against the temperature T of the thermistor is plotted.

Which graph could show the variation of I with T?


A

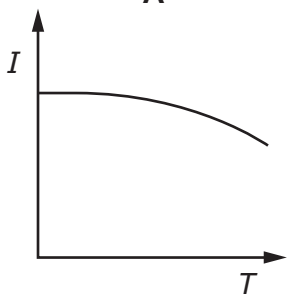

B

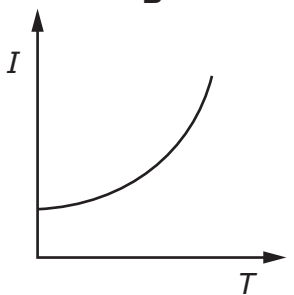

C

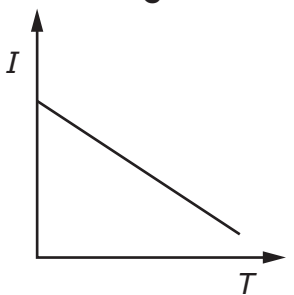

D

