36 Two resistors have a combined resistance of 34 Ω when connected in series. The same resistors have a combined resistance of 7.4 Ω when connected in parallel.

What is the resistance of one of the resistors?

A 15 Ω **B** 17 Ω **C** 23 Ω **D** 27 Ω