

33 Which circuit results in output voltage V_{out} increasing with increasing temperature?


A

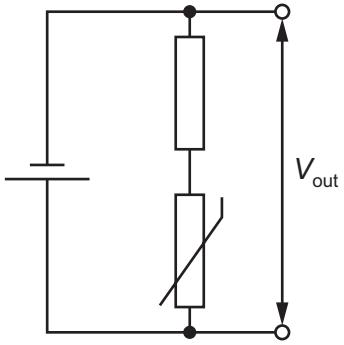

B

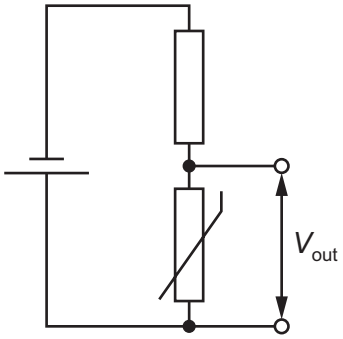

C

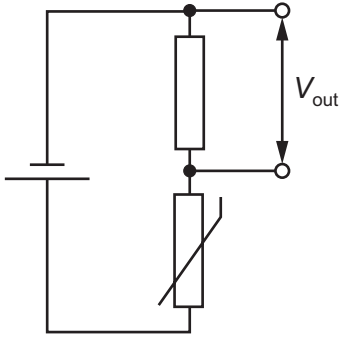

D

