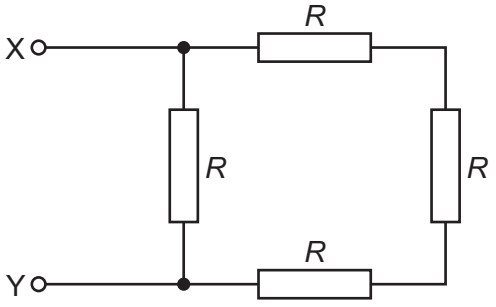
34 Four resistors, each of resistance R, are connected as shown.



The total resistance between point X and point Y is 120 Ω.

What is the magnitude of the resistance R?

A 30 Ω **B** 90 Ω **C** 160 Ω **D** 480 Ω