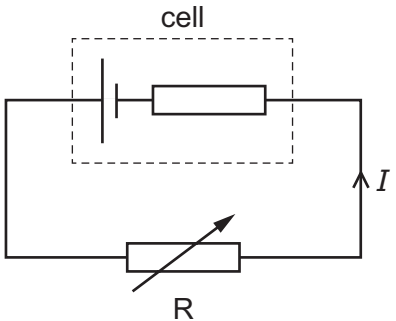
35 A cell with internal resistance is connected to a variable resistor R as shown.



The resistance of R is gradually decreased.

How do the current I and the terminal potential difference (p.d.) across the cell change?

	current I	terminal p.d. across cell
A	decreases	decreases
B	decreases	increases
C	increases	decreases
D	increases	increases