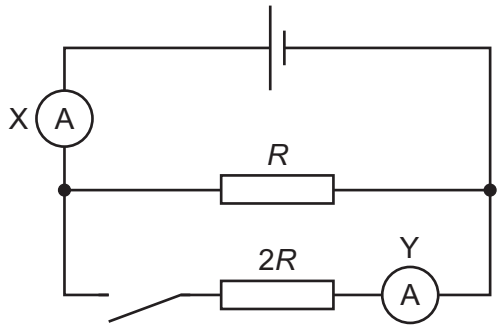
30 The diagram shows a cell of negligible internal resistance connected to a switch and two resistors of resistances R and $2R$.



The circuit also contains two ammeters X and Y.

The reading on X is 4.0 A when the switch is open.

What are the readings on X and Y after the switch is closed?

	reading on X / A	reading on Y / A
A	4.0	1.3
B	4.0	2.7
C	6.0	2.0
D	6.0	4.0