34 Which description of Kirchhoff's first law is correct?

A It considers the currents at a junction in a circuit and is a consequence of the conservation of charge.

B It considers the currents at a junction in a circuit and is a consequence of the conservation of energy.

C It considers the electromotive forces and potential differences in a circuit loop and is a consequence of the conservation of charge.

D It considers the electromotive forces and potential differences in a circuit loop and is a consequence of the conservation of energy.