
35 Two resistors of resistances r and R are connected in parallel.

The value of r is less than that of R.

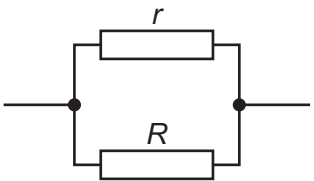

Which statement about the combined resistance of the two resistors is correct?

A It is between r and R.

B It is equal to $(r + R)$.

C It is greater than $(r + R)$.

D It is less than r.