2 A voltmeter connected across a resistor in a circuit reads 3.6 V.

What could be the current in the resistor and the resistance of the resistor?

	current	resistance
A	150 mA	0.24 kΩ
B	15 mA	2.4 kΩ
C	1.5 mA	0.24 MΩ
D	15 μA	240 kΩ