32 A power supply is connected to a component by connecting wires of total resistance 4.9 Ω.

The power supply has an output power of 3.6 W and a terminal potential difference of 12 V.

How much thermal energy is dissipated in the connecting wires in a time of 1.0 hour?

A 0.44 J **B** 29 J **C** 1.6 kJ **D** 11 kJ