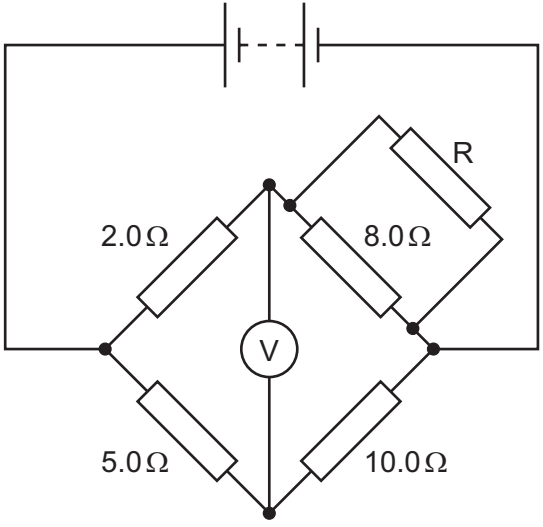
36 A circuit consists of a battery, a voltmeter and five fixed resistors, as shown.



The voltmeter reading is zero.

What is the resistance of resistor R?

A 1.1 Ω **B** 2.1 Ω **C** 4.0 Ω **D** 8.0 Ω