
37 A battery of electromotive force (e.m.f.) 6.0 V and negligible internal resistance is connected to a voltmeter and four other components, as shown.

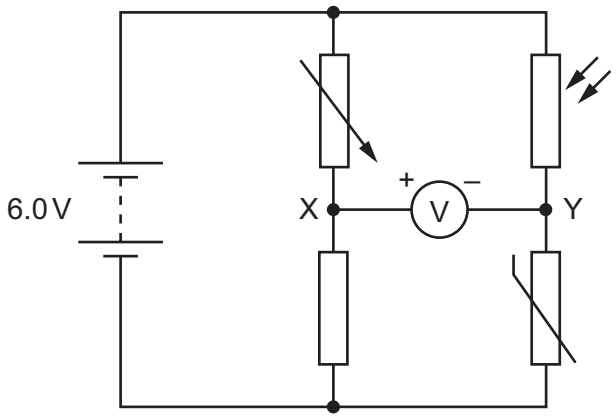The voltmeter is connected between points X and Y. The positive terminal of the voltmeter is connected to X and the negative terminal of the voltmeter is connected to Y.



Initially, the resistance of each of the four components is 1.0 kΩ.

Which change, on its own, will cause the voltmeter to show a positive reading?

A Decrease the temperature of the thermistor.

B Increase the resistance of the variable resistor.

C Reduce the intensity of light incident on the light-dependent resistor (LDR).

D Replace the fixed resistor with a 500 Ω resistor.