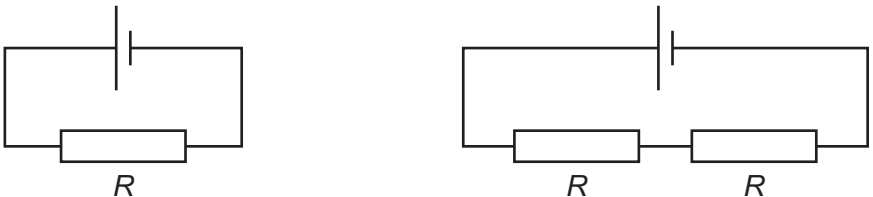
32 The diagrams show two different circuits.



The cells in each circuit have the same electromotive force (e.m.f.) and negligible internal resistance. The three resistors each have the same resistance *R*.

In the circuit on the left, the power dissipated in the resistor is *P*.

What is the total power dissipated in the circuit on the right?

A $\frac{P}{4}$ **B** $\frac{P}{2}$ **C** P **D** $2P$