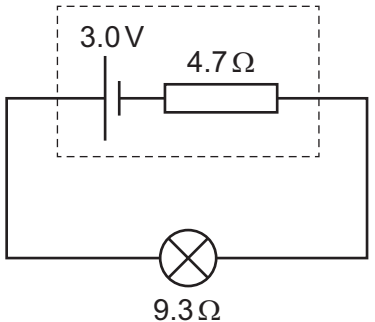
35 The diagram shows a cell of electromotive force (e.m.f.) 3.0 V and internal resistance 4.7 Ω connected across a lamp. The lamp has a resistance of 9.3 Ω.



What is the power dissipated by the internal resistance of the cell?

A 0.22 W **B** 0.43 W **C** 0.64 W **D** 1.0 W