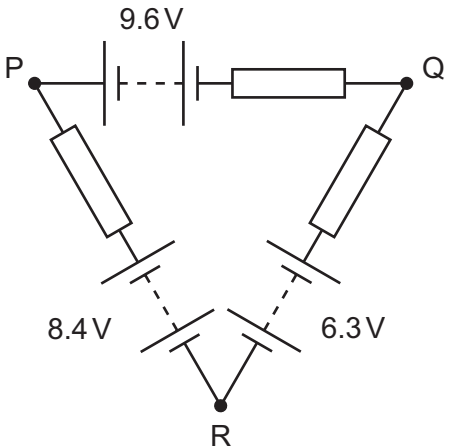
36 Three batteries and three identical resistors are connected in a circuit PQR, as shown.



The batteries have negligible internal resistance.

What is the potential difference between points P and Q?

A 1.5 V **B** 2.1 V **C** 7.1 V **D** 12.1 V