
31 In the circuit shown, the battery has an electromotive force (e.m.f.) of 6.0 V and negligible internal resistance.

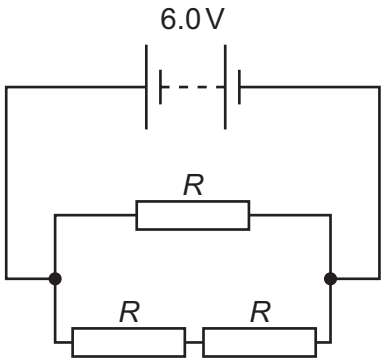The three resistors each have resistance *R*.



The total power dissipated in the resistor network is 24 W.

What is the value of *R*?

A 0.50 Ω **B** 1.0 Ω **C** 1.5 Ω **D** 2.3 Ω