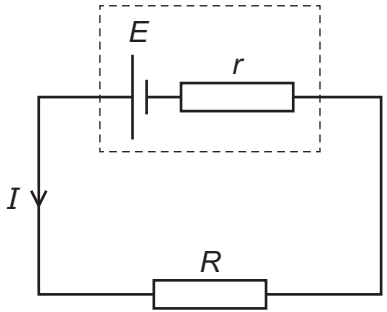
36 A circuit contains a cell of electromotive force E and internal resistance r connected to a resistor of resistance R. The current in the circuit is I.



Which equation is correct?

A $E - Ir = IR$ **B** $E = Ir - IR$ **C** $E + Ir = IR$ **D** $E = IR$