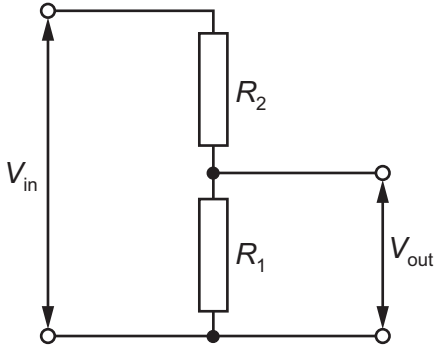
37 A potential divider consists of two resistors of resistances R_1 and R_2 connected in series across a source of potential difference (p.d.) V_{in}. The p.d. across R_1 is V_{out}.



Which changes to R_1 and R_2 will increase the value of V_{out}?

	R_1	R_2
A	doubled	doubled
B	doubled	halved
C	halved	doubled
D	halved	halved