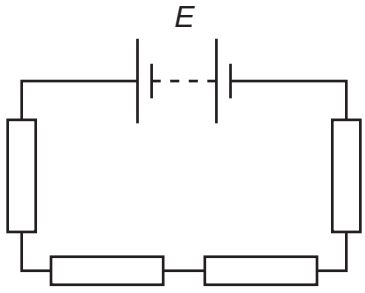
34 Some resistors and a battery of electromotive force (e.m.f.) *E* and negligible internal resistance are connected in series, as shown.



Which statement is correct?

A The e.m.f. across each resistor equals the potential difference across the battery.

B The potential difference across each resistor equals the e.m.f. *E* of the battery.

C The sum of the e.m.f.s across the resistors equals the potential difference across the battery.

D The sum of the potential differences across the resistors equals the e.m.f. *E* of the battery.