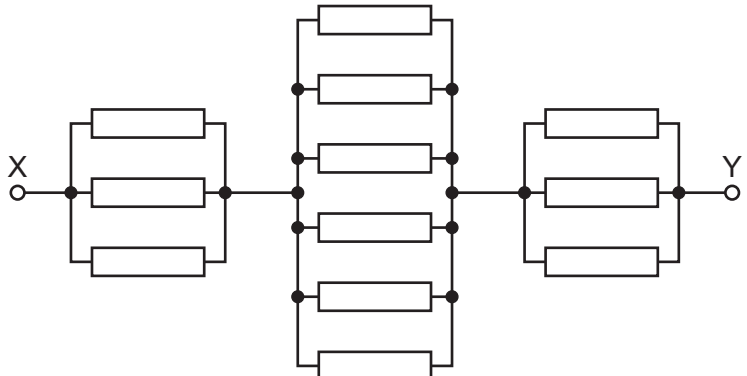
36 The diagram shows a network of resistors. Each resistor has a resistance of 6.0 Ω.



What is the total resistance of the network between points X and Y?

A 3.0 Ω **B** 5.0 Ω **C** 7.2 Ω **D** 18 Ω